

Video Lecture NotesLab 5 Last Question (Loom)

- Gained insight on specified resistance looking for most linear region
- Voltage calculation depends on spot where measured spot between resistor and zener diode
- be careful of diode choice (increase reverse biased current)

Lab 4 Tutorial - Gain Calculation

- Chapter 2 slide 2 for further gain study
- $j$  imaginary # therefore  $\sqrt{\quad}$  must be introduced (very fundamental)

$\left( \frac{R_2}{R_1} \right)$  Ratio derived formula  

$$\frac{\left( \frac{R_2}{R_1} \right)}{\sqrt{1 + (2\pi f C R_2)^2}} = 1$$

$$0\text{db} = \text{input} = \text{output}$$